


Chapter 5 Impedance Matching and Tuning



- The matching network is *ideally lossless*, and is usually designed so that the impedance seen looking into the matching network is Z_0 .
- Only if $\text{Re}[Z_L] \neq 0$, a matching network can always be found.
- The quarter-wave impedance transformer is for real load.
- Important factors in selecting matching networks:
(1)complexity, (2)bandwidth, (3)implementation, (4)adjustability.

1


Review of Smith Chart

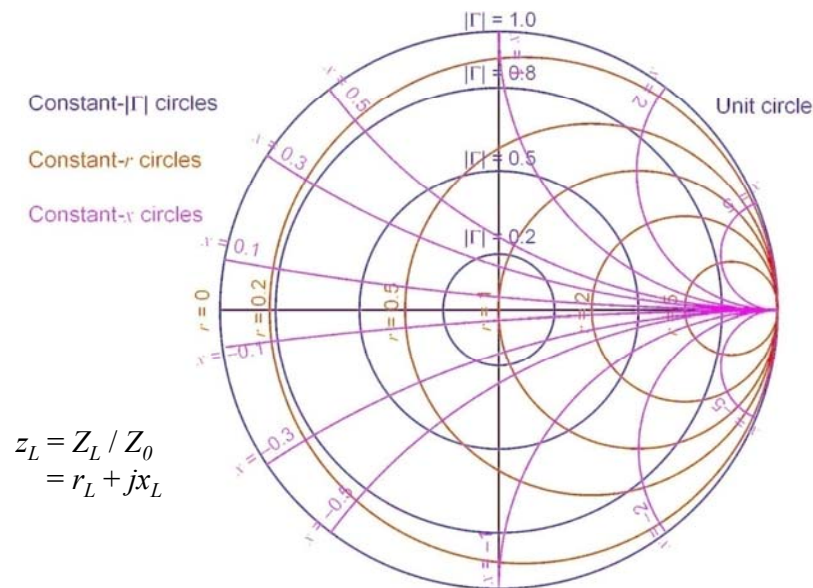

2

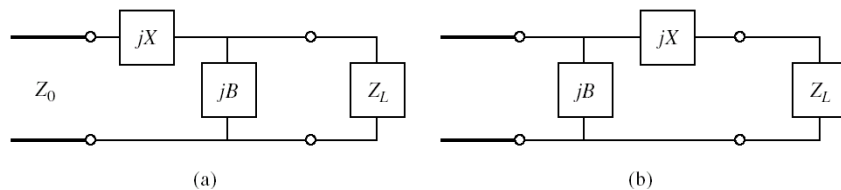5.1 Lumped Element Matching (L-networks)

L-type or *L*-network matching is the simplest matching network.



(1) $z_L = Z_L / Z_0$ is inside the $r=1$ circle ($r_L > 1$).

(2) Z_L is shunt with jB , then series with jX .

(1) $z_L = Z_L / Z_0$ is outside the $r=1$ circle ($r_L < 1$).

(2) Z_L is series with jB , then shunt with jX .

3


Analytical Solutions ($r_L > 1$)

- When $r_L > 1$, let $Z_L = R_L + jX_L$ and $z_L = Z_L / Z_0 = r_L + jx_L$

$$Z_{in} = jX + \frac{1}{jB + \frac{1}{R_L + jX_L}} \equiv Z_0$$

$$\begin{cases} B(XR_L - X_L Z_0) = R_L - Z_0 \\ X(1 - BX_L) = BZ_0 R_L - X_L \end{cases}$$
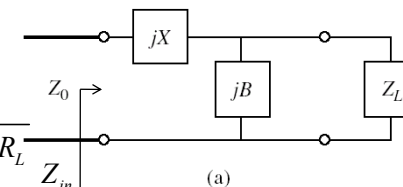
$$\Rightarrow \begin{cases} B = \frac{X_L \pm \sqrt{\frac{R_L}{Z_0} \sqrt{R_L^2 + X_L^2} - Z_0 R_L}}{R_L^2 + X_L^2} \\ X = \frac{1}{B} + \frac{X_L Z_0}{R_L} - \frac{Z_0}{BR_L} \end{cases}$$



- Note that when $r_L > 1$, the square root in B has real results.

4

Analytical Solutions ($r_L < 1$)


- When $r_L < 1$, let $Z_L = R_L + jX_L$ and $z_L = Z_L / Z_0 = r_L + jx_L$

$$\frac{1}{Z_{in}} = jB + \frac{1}{R_L + j(X + X_L)} \equiv \frac{1}{Z_0}$$

$$BZ_0(X + X_L) = Z_0 - R_L$$

$$(X + X_L) = BZ_0R_L$$
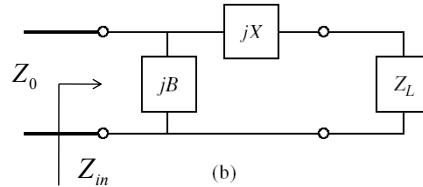
$$\Rightarrow \begin{cases} B = \pm \frac{\sqrt{(Z_0 - R_L)/R_L}}{Z_0} \\ X = -X_L \pm \sqrt{R_L(Z_0 - R_L)} \end{cases}$$




- Two analytical solutions are physically realizable.
- One of the two solutions may result in smaller reactive elements, and may have better matching, bandwidth, or better SWR on the line.

5

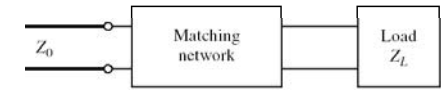Example 5.1 L-Section Impedance Matching

$Z_L = 200 - j100 \Omega$, $Z_0 = 100 \Omega$,
 $f = 500 \text{ MHz}$, $z_L = Z_L / Z_0 = 2 - j1$,
 $r_L = 2 > 1$ inside the $r = 1$ circle.



Exact solutions:

$$B = \frac{X_L \pm \sqrt{\frac{R_L}{Z_0} \sqrt{R_L^2 + X_L^2} - R_L Z_0}}{R_L^2 + X_L^2}$$

$$= \frac{-100 \pm \sqrt{2} \sqrt{200^2 + 100^2} - 100 \times 200}{200^2 + 100^2} = \left\{ \begin{array}{l} 2.899 \times 10^{-3} \Omega^{-1} \\ -6.899 \times 10^{-3} \Omega^{-1} \end{array} \right\}$$

$$X = \frac{1}{B} + \frac{X_L Z_0}{R_L} - \frac{Z_0}{B R_L} = \left\{ \begin{array}{l} 122.47 \Omega \\ -122.47 \Omega \end{array} \right\}$$


6

Example 5.1 L-Section Impedance Matching

The two solutions:


$$(1) C = \frac{B}{\omega} = \frac{2.899 \times 10^{-3}}{2\pi \times 500 \times 10^6} = 0.9228 \text{ pF}$$
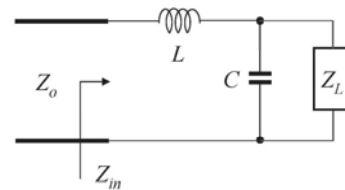
$$L = \frac{X}{\omega} = \frac{122.47}{2\pi \times 500 \times 10^6} = 38.98 \text{ nH}$$



$$(2) C = -\frac{1}{X\omega} = \frac{1}{122.47 \times 2\pi \times 500 \times 10^6} = 2.599 \text{ pF}$$


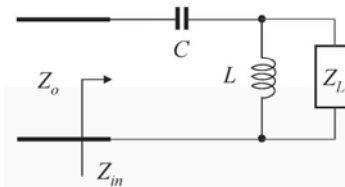
$$L = -\frac{1}{B\omega} = \frac{1}{6.899 \times 10^{-3} \times 2\pi \times 500 \times 10^6} = 46.14 \text{ nH}$$



7


Example 5.1 L-Section Impedance Matching

The two solutions:

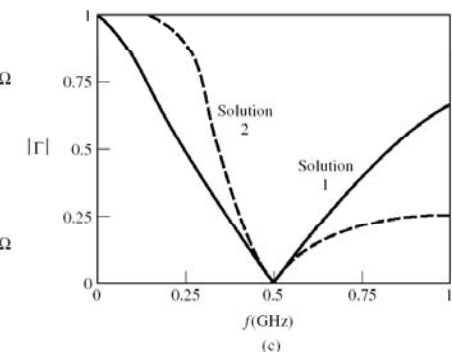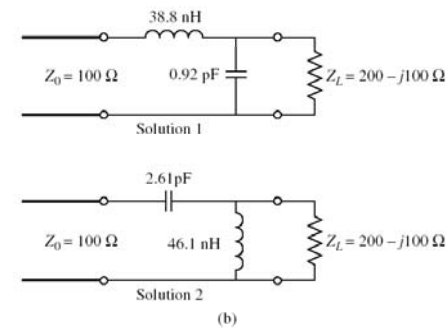


8

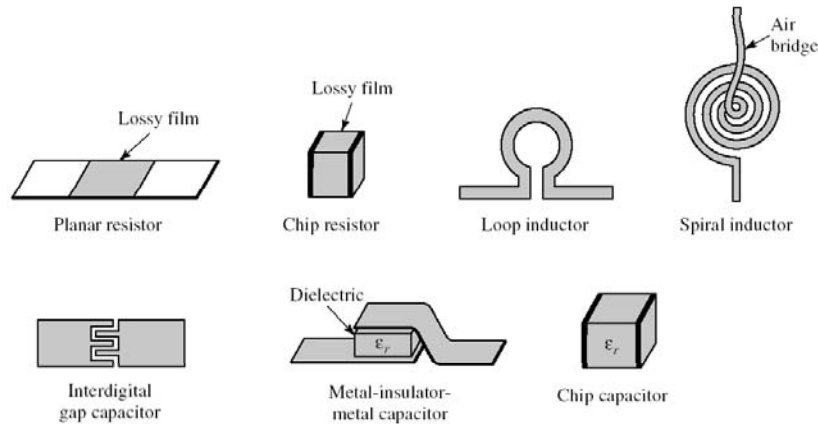Lumped Elements for Microwave Integrated Circuits (MICs)



9

5.2 Single-Stub Tuning

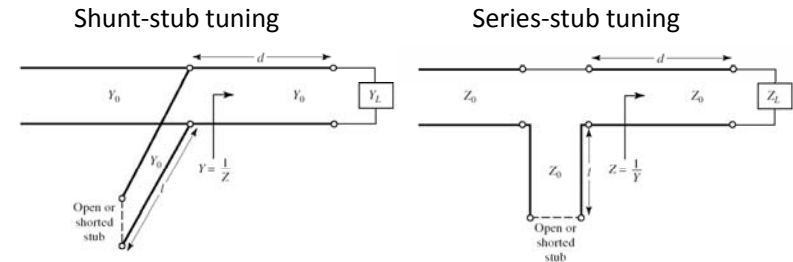

- No lumped element is required. Convenient for MIC fabrication.
- Characteristic impedances of the lines and the stub can be different.
- **Keep the matching stub as close as possible to the load.**
- Solution procedure for *shunt-stub* and *series-stub* tunings.
 - (1) Locate z_L (y_L) on the Smith Chart.
 - (2) Move along the const- Γ circle with $2d/\lambda$ wavelengths to reach the $g = 1$ ($r = 1$) circle.
 - (3) Shunt with a susceptance or series with a reactance to cancel the imaginary part.

10

Shunt-Stub Tuning Analytical Solution

$$Z_{in}|_{no\ stub} = Z_0 \frac{Z_L + jZ_0 t}{Z_0 + jZ_L t} \Big|_{t=\tan \beta d} = \frac{1}{Y_0} \frac{R_L + j(X_L + Z_0 t)}{Z_0 - X_L t + jR_L t} \equiv \frac{1}{G_{in} + jB_{in}}$$

$$G_{in} = \frac{R_L(1+t^2)}{R_L^2 + (X_L + Z_0 t)^2}, \quad B_{in} = Y_0 \frac{R_L^2 t - (Z_0 - X_L t)(Z_0 t + X_L)}{R_L^2 + (X_L + Z_0 t)^2}$$

$$G_{in} = Y_0 \Rightarrow Z_0 R_L (1+t^2) = R_L^2 + (X_L + Z_0 t)^2 \quad \text{real part}$$

$$\text{If } R_L = Z_0, \text{ and } t = \tan \beta d = -\frac{X_L}{2Z_0}$$

$$\Rightarrow \frac{d}{\lambda} = \begin{cases} \frac{1}{2\pi} \tan^{-1} \left(-\frac{X_L}{2Z_0} \right), & X_L < 0 \\ \frac{1}{2\pi} \left[\pi + \tan^{-1} \left(-\frac{X_L}{2Z_0} \right) \right], & X_L > 0 \end{cases}$$

11

Shunt-Stub Tuning Analytical Solution

If $R_L \neq Z_0$,

$$t = \frac{X_L Z_0 \pm \sqrt{(X_L Z_0)^2 - Z_0(R_L - Z_0)(R_L Z_0 - R_L^2 - X_L^2)}}{Z_0(R_L - Z_0)}$$

$$X_L \pm \sqrt{\left(\frac{R_L}{Z_0}\right)^2 [(R_L - Z_0)^2 + X_L^2]}$$

$$= \frac{R_L - Z_0}{R_L - Z_0}$$

Let the stub susceptance B_{stub} (or B_s) = $-B_{in}$,

here $t = \tan \beta l$

(a) open-stub: $Z_{stub} = -jZ_0/t$ and $Y_{stub} = jY_0 t = jB_{stub} \equiv jB_s$

$$\frac{l_o}{\lambda} = \frac{1}{2\pi} \tan^{-1} \left(\frac{B_s}{Y_0} \right) = -\frac{1}{2\pi} \tan^{-1} \left(\frac{B_{in}}{Y_0} \right)$$

(b) Short-stub: $Z_{stub} = jZ_0 t$ and $Y_{stub} = -jY_0/t = jB_{stub} \equiv jB_s$

$$\frac{l_s}{\lambda} = -\frac{1}{2\pi} \tan^{-1} \left(\frac{Y_0}{B_s} \right) = \frac{1}{2\pi} \tan^{-1} \left(\frac{Y_0}{B_{in}} \right)$$

If $l_o < 0$ or $l_s < 0$, $\lambda/2$ must be added to have a realistic result.

12

Example 5.2 Shunt Single-Stub Tuning

Match $Z_L = 15 + j10 \Omega$ to a $50\text{-}\Omega$ line. Use a shunt open-stub.

Sol: $R_L \neq Z_0$,


$$t = \frac{X_L \pm \sqrt{\left(\frac{R_L}{Z_0}\right)^2 [(R_L - Z_0)^2 + X_L^2]}}{R_L - Z_0} = -\frac{10 \pm \sqrt{397.5}}{35}$$

$$t_1 = -\frac{10 + \sqrt{397.5}}{35} \Rightarrow \frac{d}{\lambda} = \frac{1}{2\pi} (\pi + \tan^{-1} t_1) = 0.387$$

$$\Rightarrow B_{in} = \dots \Rightarrow \frac{l_o}{\lambda} = -\frac{1}{2\pi} \tan^{-1} \left(\frac{B_{in}}{Y_0} \right)$$

$$t_2 = -\frac{10 - \sqrt{397.5}}{35} \Rightarrow \frac{d}{\lambda} = \frac{1}{2\pi} \tan^{-1} t_2 = 0.044$$
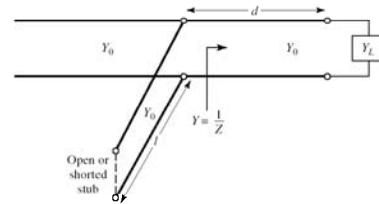
$$\Rightarrow B_{in} = \dots \Rightarrow \frac{l_o}{\lambda} = -\frac{1}{2\pi} \tan^{-1} \left(\frac{B_{in}}{Y_0} \right)$$




13

Example 5.2 Shunt Single-Stub Tuning (Cont'd)

Use a shunt open-stub to match $Z_L = 15 + j10 \Omega$ line.

Solution 1:


Solution 2:

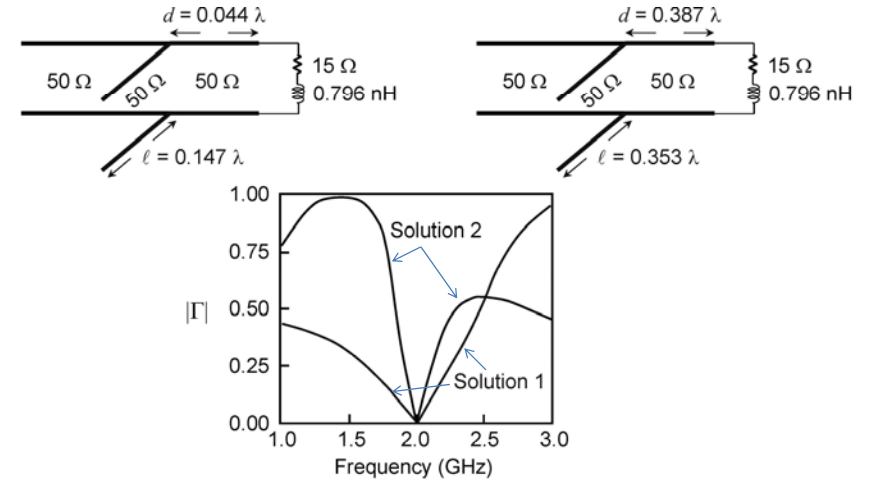

14

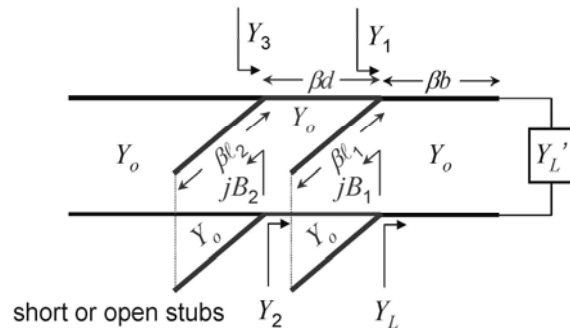5.3 Double-Stub Tuning – Analytical Solution


- In single-stub tuning, the length d is not tunable.
- If this causes difficulty in circuit implementation, use double-stub tuning.



$$Y_L = Y_0 \frac{Y_L' + jY_0 \tan \beta b}{Y_0 + jY_L' \tan \beta b} \equiv G_L + jB_L$$

15

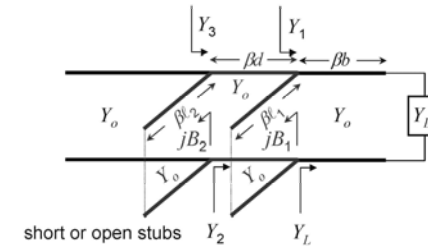5.3 Double-Stub Tuning – Analytical Solution



$$Y_1 = G_L + j(B_L + B_1)$$

$$Y_2 = Y_0 \frac{G_L + j(B_L + B_1 + Y_0 t)}{Y_0 + j t (G_L + j B_L + j B_1)}, \quad t = \tan \beta d$$

$$\text{Re}[Y_2] = Y_0, \quad \text{Im}[Y_2] = -B_2$$

$$G_L^2 - Y_0 \frac{1+t^2}{t^2} G_L + \frac{(Y_0 - B_L t - B_1 t)^2}{t^2} = 0$$

$$G_L = Y_0 \frac{1+t^2}{t^2} \left\{ 1 \pm \sqrt{1 - \frac{4t^2(Y_0 - B_L t - B_1 t)^2}{Y_0(1+t^2)^2}} \right\}$$

$$0 \leq 4t^2(Y_0 - B_L t - B_1 t)^2 \leq Y_0^2(1+t^2)^2$$

$$0 \leq G_L \leq Y_0 \frac{1+t^2}{2t^2} = \frac{Y_0}{\sin^2 \beta d}$$

G_L has an upper limit.

Given d , one can obtain:

$$B_1 = -B_L + \frac{Y_0 + \sqrt{(1+t^2)G_L Y_0 - G_L^2 t^2}}{t}$$

$$B_1 = Y_0 \frac{G_L \pm \sqrt{(1+t^2)G_L Y_0 - G_L^2 t^2}}{t}$$


$$\frac{l_o}{\lambda} = \frac{1}{2\pi} \tan^{-1} \left(\frac{B}{Y_0} \right), \quad B = B_1, B_2$$

$$\frac{l_s}{\lambda} = \frac{1}{2\pi} \tan^{-1} \left(\frac{Y_0}{B} \right), \quad B = B_1, B_2$$

16

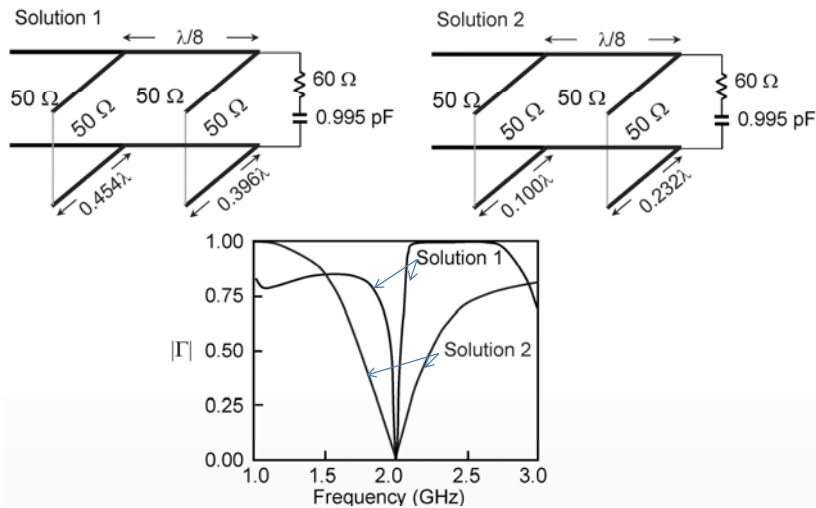Example 5.4 Double-Stub Tuning - Performance


Use double-stub matching scheme to match $Z_L = 60 - j80\Omega$ at 2.0 GHz to a 50- Ω line.



17

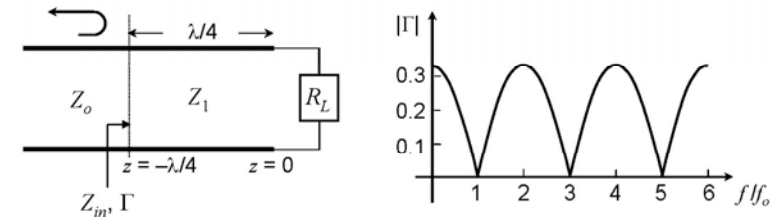5.4 The Quarter-Wave Transformer

- A single-section transformer may suffice for a *narrow-band* impedance matching.
- Single-section quarter-wave impedance matching $\lambda = \lambda_0 / 4$ at the desired frequency. (See Chap 2)



Bandwidth of the Matching Transformer

$$\Delta\theta = 2(\pi/2 - \theta_m)$$

$$\theta_m: \frac{1}{\Gamma_m^2} = 1 + \frac{4Z_0 Z_L}{(Z_0 - Z_L)^2} \sec^2 \theta_m$$



$$\theta \equiv \frac{\pi f}{2 f_0}, \quad \theta_m = \frac{\pi f_m}{2 f_0}, \quad f_m = \frac{2\theta_m}{\pi} f_0$$

$$\cos \theta_m = \frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}} \frac{2\sqrt{Z_0 Z_L}}{|Z_0 - Z_L|}$$

Fractional bandwidth:

$$\frac{\Delta f}{f_0} = \frac{2(f_0 - f_m)}{f_0} = 2 - \frac{4\theta_m}{\pi}$$

$$= 2 - \frac{4}{\pi} \left(\cos^{-1} \left[\frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}} \frac{2\sqrt{Z_0 Z_L}}{|Z_0 - Z_L|} \right] \right)$$

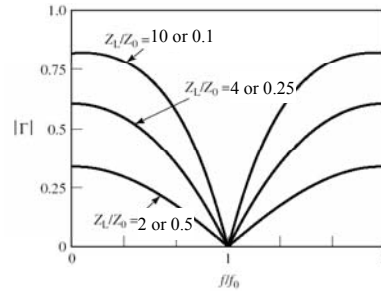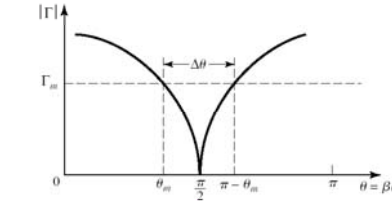

L

Example 5.5

Single-Section Quarter-Wave Transformer Bandwidth

$$Z_L = 10 \Omega, Z_0 = 100 \Omega, SWR = 1.2$$

Sol:


$$Z_1 = \sqrt{Z_0 Z_L} = 31.6 \Omega$$

$$\Gamma_m = \frac{SWR - 1}{SWR + 1} = 0.1$$

$$SWR = \frac{V_{\max}}{V_{\min}} = \frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} = \frac{1 + \Gamma}{1 - \Gamma}$$

$$\frac{\Delta f}{f_0} = 2 - \frac{4}{\pi} \left(\cos^{-1} \left[\frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}} \frac{2\sqrt{Z_0 Z_L}}{|Z_0 - Z_L|} \right] \right)$$
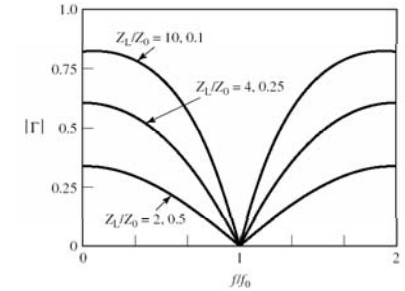
$$= 2 - \frac{4}{\pi} \left(\cos^{-1} \left[\frac{0.1}{\sqrt{0.99}} \frac{2 \times 31.6}{90} \right] \right) = 2 - \frac{6}{\pi} \approx 9\%$$




22

5.5 Theory of Small Reflections

- For applications requiring more bandwidth than that a single quarter-wave section can provide, multi-section transformers can be used.

(1) Single-Section Transformer

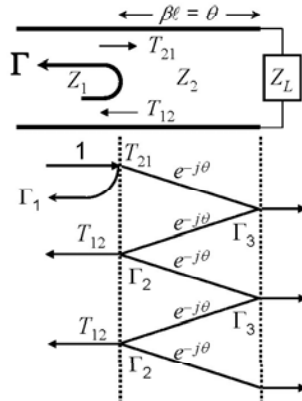

$$\Gamma_1 = \frac{Z_2 - Z_1}{Z_2 + Z_1} = -\Gamma_2$$

$$\Gamma_3 = \frac{Z_L - Z_2}{Z_L + Z_2}$$

$$T_{21} = 1 + \Gamma_1 = \frac{2Z_2}{Z_2 + Z_1}$$

$$T_{12} = 1 + \Gamma_2 = \frac{2Z_1}{Z_2 + Z_1}$$

23

5.5 Theory of Small Reflections

(1) Multi-Reflections


$$\Gamma = \Gamma_1 + T_{12} T_{21} \Gamma_3 e^{-j2\theta} + T_{12} T_{21} \Gamma_3^2 \Gamma_2 e^{-j4\theta} + \dots$$

$$= \Gamma_1 + T_{12} T_{21} \Gamma_3 e^{-j2\theta} (1 + \Gamma_3 \Gamma_2 e^{-j2\theta} + (\Gamma_3 \Gamma_2)^2 e^{-j4\theta} + \dots) \Gamma_1$$

$$= \Gamma_1 + T_{12} T_{21} \Gamma_3 e^{-j2\theta} \sum_{n=0}^{\infty} (\Gamma_3 \Gamma_2)^n e^{-j2n\theta}$$


$$= \Gamma_1 + \frac{T_{12} T_{21} \Gamma_3 e^{-j2\theta}}{1 - \Gamma_3 \Gamma_2 e^{-j2\theta}} = \frac{\Gamma_1 + \Gamma_3 e^{-j2\theta}}{1 + \Gamma_1 \Gamma_3 e^{-j2\theta}}$$

- If $|\Gamma_1 \Gamma_3|$ is small, $\Gamma \approx \Gamma_1 + \Gamma_3 e^{-j2\theta}$
- $\Gamma \approx$ the reflection from the initial discontinuity between Z_1 and Z_2 + the first reflection from the discontinuity between Z_2 and Z_L .

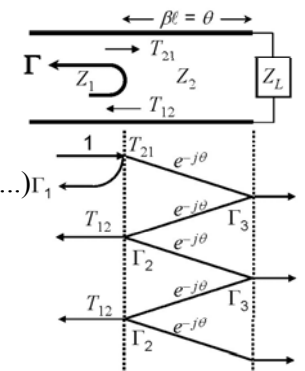

24

Multisection Transformer

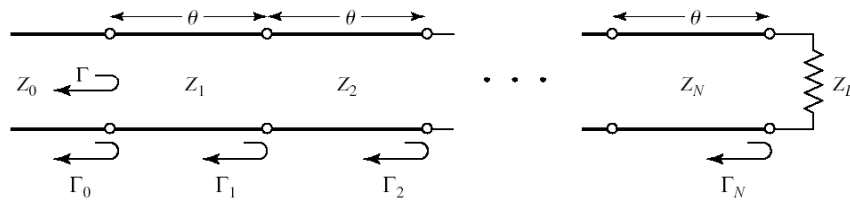


- N commensurate (equal-length) sections of transmission lines. Let the total reflection be Γ .
- Assume that all Z_n increase or decrease monotonically, Z_L is real, and “The theory of small reflections” holds.

- It can be validated that

$$\Gamma_0 = \frac{Z_1 - Z_0}{Z_1 + Z_0}, \quad \Gamma_1 = \frac{Z_2 - Z_1}{Z_2 + Z_1}, \quad \Gamma_2 = \frac{Z_3 - Z_2}{Z_3 + Z_2}, \quad \dots \quad \Gamma_N = \frac{Z_L - Z_N}{Z_L + Z_N}$$

25

Multisection Transformer

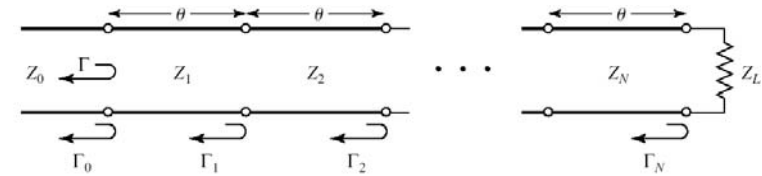

$$\begin{aligned} \Gamma &\approx \Gamma_0 + \Gamma_1 e^{-j2\theta} + \Gamma_2 e^{-j4\theta} + \dots + \Gamma_N e^{-j2N\theta} \\ &= e^{-jN\theta} [\Gamma_0 (e^{jN\theta} + e^{-jN\theta}) + \Gamma_1 (e^{j(N-2)\theta} + e^{-j(N-2)\theta}) + \dots] \quad (\text{if symmetry}) \\ &= 2e^{-jN\theta} \begin{cases} [\Gamma_0 \cos N\theta + \Gamma_1 \cos(N-2)\theta + \dots + \Gamma_{N/2}], & N = \text{even} \\ [\Gamma_0 \cos N\theta + \Gamma_1 \cos(N-2)\theta + \dots + \Gamma_{(N-1)/2} \cos \theta], & N = \text{odd} \end{cases} \end{aligned}$$

- We can synthesize any desired $|\Gamma|$ response as a function of frequency or θ , by properly choosing the Γ_n 's and enough number of sections N .
- The most commonly used passband responses are:
 - (1) Binomial or maximally flat response, and
 - (2) Chebyshev or equal-ripple response.

26

How to Find the Corresponding Reflection?

Theory of Small Reflection:

$$\Gamma(\theta) \approx \Gamma_0 + \Gamma_1 e^{-j2\theta} + \Gamma_2 e^{-j4\theta} + \dots + \Gamma_N e^{-j2N\theta}$$

Binomial Multi-Section Transformer:

$$\Gamma(\theta) = A(1 + e^{-j2\theta})^N$$

Chebyshev Multi-Section Transformer:

$$\Gamma(\theta) = AT_n(\sec \theta_m \cos \theta)$$

27

5.6 Binomial Multisection Matching Transformer

- Maximally flat response: the response is as flat as possible near the design frequency. Also called Binomial matching transformer.
- Let $\Gamma(\theta) = A(1 + e^{-j2\theta})^N \Leftarrow$ Assumed artificially

$$|\Gamma(\theta)| = 2^N |A| |\cos \theta|^N$$

$$\Gamma(0) = 2^N A = \frac{Z_L - Z_0}{Z_L + Z_0} \Rightarrow A = \frac{\Gamma(0)}{2^N}$$

$$\Gamma(\theta) = A(1 + e^{-j2\theta})^N = A \sum_{n=0}^N C_n^N e^{-j2n\theta}, \quad C_n^N = \frac{N!}{(N-n)!n!}$$

$$= \Gamma_0 + \Gamma_1 e^{-j2\theta} + \Gamma_2 e^{-j4\theta} + \dots + \Gamma_N e^{-j2N\theta}$$


$$\Gamma_n = AC_n^N = \frac{\Gamma(0)}{2^N} C_n^N$$

$N!$ ("enn factorial")
"Four factorial" is written as "4!"

Properly configure the impedances to synthesize the needed reflections Γ_n .

28

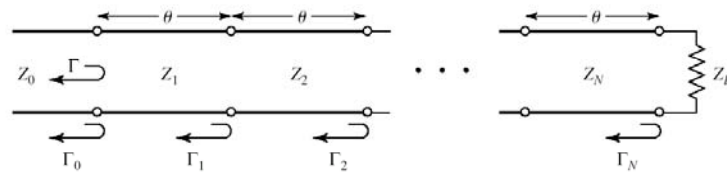Binomial Multisection Matching Transformer



$$\Gamma_n = \frac{Z_{n+1} - Z_n}{Z_{n+1} + Z_n} \approx \frac{1}{2} \ln \frac{Z_{n+1}}{Z_n}, \quad \ln x \approx 2 \frac{x-1}{x+1}, \quad |x-1| \ll 1$$

$$\ln \frac{Z_{n+1}}{Z_n} \approx 2\Gamma_n = 2AC_n^N = \frac{1}{2^{N-1}} C_n^N \frac{Z_L - Z_0}{Z_L + Z_0} \approx \frac{1}{2^N} C_n^N \ln \frac{Z_L}{Z_0}$$

$$\frac{Z_{n+1}}{Z_n} \approx \left(\frac{Z_L}{Z_0} \right)^{C_n^N / 2^N}$$

- Exact results for Z_{n-1} / Z_0 for $N = 2$ thru 6 are given in Table 5.1.

29

Binomial Transformer Design Table 5.1

TABLE 5.1 Binomial Transformer Design

Z_L/Z_0	$N = 2$		$N = 3$			$N = 4$			
	Z_1/Z_0	Z_2/Z_0	Z_1/Z_0	Z_2/Z_0	Z_3/Z_0	Z_1/Z_0	Z_2/Z_0	Z_3/Z_0	Z_4/Z_0
1.0	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000
1.5	1.1067	1.3554	1.0520	1.2247	1.4259	1.0257	1.1351	1.3215	1.4624
2.0	1.1892	1.6818	1.0907	1.4142	1.8337	1.0444	1.2421	1.6102	1.9150
3.0	1.3161	2.2795	1.1479	1.7321	2.6135	1.0718	1.4105	2.1269	2.7990
4.0	1.4142	2.8285	1.1907	2.0000	3.3594	1.0919	1.5442	2.5903	3.6633
6.0	1.5651	3.8336	1.2544	2.4495	4.7832	1.1215	1.7553	3.4182	5.3500
8.0	1.6818	4.7568	1.3022	2.8284	6.1434	1.1436	1.9232	4.1597	6.9955
10.0	1.7783	5.6233	1.3409	3.1623	7.4577	1.1613	2.0651	4.8424	8.6110


Z_L/Z_0	$N = 5$					$N = 6$					
	Z_1/Z_0	Z_2/Z_0	Z_3/Z_0	Z_4/Z_0	Z_5/Z_0	Z_1/Z_0	Z_2/Z_0	Z_3/Z_0	Z_4/Z_0	Z_5/Z_0	Z_6/Z_0
1.0	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000
1.5	1.0128	1.0790	1.2247	1.3902	1.4810	1.0064	1.0454	1.1496	1.3048	1.4349	1.4905
2.0	1.0220	1.1391	1.4142	1.7558	1.9569	1.0110	1.0790	1.2693	1.5757	1.8536	1.9782
3.0	1.0354	1.2300	1.7321	2.4390	2.8974	1.0176	1.1288	1.4599	2.0549	2.6577	2.9481
4.0	1.0452	1.2995	2.0000	3.0781	3.8270	1.0225	1.1661	1.6129	2.4800	3.4302	3.9120
6.0	1.0596	1.4055	2.4495	4.2689	5.6625	1.0296	1.2219	1.8573	3.2305	4.9104	5.8275
8.0	1.0703	1.4870	2.8284	5.3800	7.4745	1.0349	1.2640	2.0539	3.8950	6.3291	7.7302
10.0	1.0789	1.5541	3.1623	6.4346	9.2687	1.0392	1.2982	2.2215	4.5015	7.7030	9.6228

30

Example Binomial Transformer Design

Z_L/Z_0	$N=5$				
	Z_1/Z_0	Z_2/Z_0	Z_3/Z_0	Z_4/Z_0	Z_5/Z_0
1.0	1.0000	1.0000	1.0000	1.0000	1.0000
1.5	1.0128	1.0790	1.2247	1.3902	1.4810
2.0	1.0220	1.1391	1.4142	1.7558	1.9569
3.0	1.0354	1.2300	1.7321	2.4390	2.8974
4.0	1.0452	1.2995	2.0000	3.0781	3.8270
6.0	1.0596	1.4055	2.4495	4.2689	5.6625
8.0	1.0703	1.4870	2.8284	5.3800	7.4745
10.0	1.0789	1.5541	3.1623	6.4346	9.2687

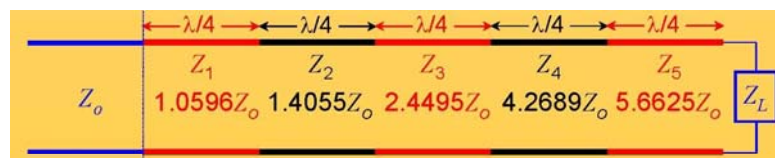- A 5th order binomial transformer for $Z_L = 6Z_0$




- Also note that $\frac{6}{5.6625} = 1.0596$, $\frac{6}{4.2689} = 1.4055$

31

Example Binomial Transformer Design $Z_L/Z_0 < 1$

Z_L/Z_0	$N=5$				
	Z_1/Z_0	Z_2/Z_0	Z_3/Z_0	Z_4/Z_0	Z_5/Z_0
6.0000	1.0596	1.4055	2.4495	4.2689	5.6625
0.1667	0.9438	0.7115	0.4082	0.2343	0.1766

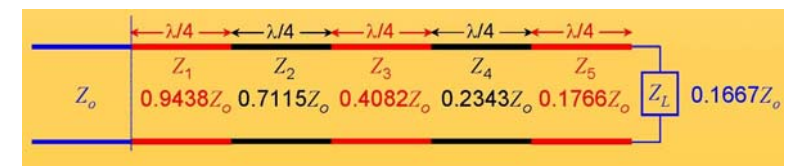- A 5th order binomial transformer for $Z_L = Z_0 / 6$



32

Bandwidth of the Binomial Transformer

$\Gamma_m = 2^N |A| \cos^N \theta_m$, i.e, tolerable $\max |\Gamma_m|$ over the passband.

$$\theta_m = \cos^{-1} \left(\frac{1}{2} \left(\frac{\Gamma_m}{|A|} \right)^{1/N} \right)$$

$$\frac{\Delta f}{f_0} = \frac{2(f_0 - f_m)}{f_0} = 2 - \frac{4\theta_m}{\pi} = 2 - \frac{4}{\pi} \cos^{-1} \left(\frac{1}{2} \left(\frac{\Gamma_m}{|A|} \right)^{1/N} \right)$$

Example 5.6 $N = 3$, $Z_L = 2Z_0 = 100 \Omega$, find the BW for $\Gamma_m = 0.05$.

Sol: From Table 5.1, the required impedance Z_n can be found to be


$$Z_1 = 54.5 \Omega, \quad Z_2 = 70.7 \Omega, \quad Z_3 = 91.7 \Omega$$

$$A = 2^{-N} \Gamma(0) = \frac{1}{8} \frac{100 - 50}{100 + 50} = 0.4167$$

$$\frac{\Delta f}{f_0} = 2 - \frac{4}{\pi} \cos^{-1} \left[\frac{1}{2} \left(\frac{0.05}{0.4167} \right)^{\frac{1}{3}} \right] = 70\%$$

33

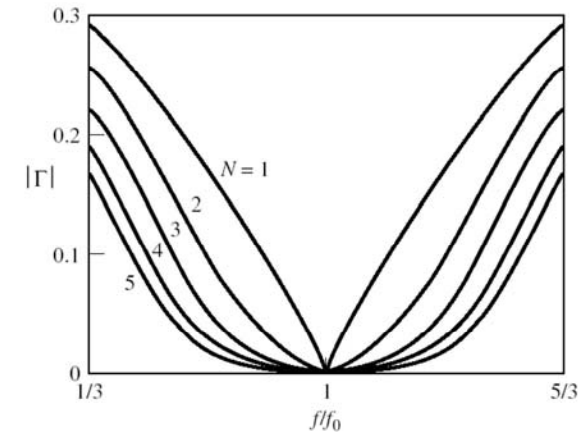Binomial Transformer's Frequency Response



Reflection coefficient magnitude versus frequency for multisection binomial matching transformer of Ex. 5.6 with $Z_L = 2Z_0 = 100 \Omega$ and $\Gamma_m = 0.05$.

34

DIY

Example (2nd Midterm)

Design a Butterworth transformer of $N = 2$ for $Z_L = 4Z_0$. Let Γ_0 , Γ_1 and Γ_L be respectively the reflection coefficients at the $Z_0 - Z_1$, $Z_1 - Z_2$ and $Z_2 - Z_L$ junctions, and $\Gamma_0 = \Gamma_L$. (a) Based on the “theory of small reflection,” find the Γ_{in} terms of Γ_0 , Γ_1 and θ . (b) If $\Gamma_{in} = 0$ and $\partial|\Gamma_{in}|/\partial\theta = 0$ are required when $\theta = \lambda/4$, find a and b .

$$|\Gamma_{in}| \approx |\Gamma_0 + \Gamma_1 e^{-j2\theta} + \Gamma_2 e^{-j4\theta}| = |2\Gamma_0 \cos 2\theta + \Gamma_1|$$

$$2\Gamma_0 \cos \left(2 \times \frac{\pi}{2} \right) + \Gamma_1 = 0 \Rightarrow \Gamma_1 = -2\Gamma_0$$

$$\frac{\partial|\Gamma_{in}|}{\partial\theta} = -4\Gamma_0 \sin 2\theta = 0$$

$$\frac{a-1}{a+1} = \frac{4-b}{4+b} \Rightarrow 4a + ab - 4 - b = 4a + 4 - ab - b \Rightarrow ab = 4$$


$$\frac{b-a}{b+a} = 2 \frac{a-1}{a+1} \Rightarrow ab - a^2 + b - a = 2(ab + a^2 - b - a) \Rightarrow a^3 - \frac{1}{3}a^2 + \frac{4}{3}a - 4 = 0$$

$$r = \frac{1}{6} \left(-\frac{4}{9} + 12 \right) + \frac{1}{27} \frac{1}{27} = 1.9273, \quad q = \frac{4-1/9}{9} = \frac{35}{81} = 0.4321$$

$$\sqrt[3]{r + \sqrt{q^3 + r^2}} = 1.5707, \quad \sqrt[3]{r - \sqrt{q^3 + r^2}} = -0.2751$$

$$a = \frac{1}{9} + 1.5707 - 0.2751 = 1.4067$$

$$b = 4/a = 2.8435$$

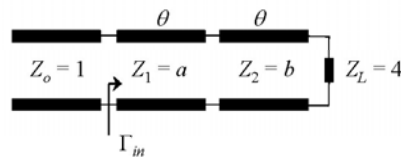

The “exact” solution in Table 5.1 is $a = 1.4142$ and $b = 2.8285$. The error is from the approximation used in the “theory of small reflection.”

35

5.7 Chebyshev Multisection Matching Transformers

Chebyshev polynomials:

Recurrence formula:

$$T_0(x) = 1$$


$$T_1(x) = x$$

$$T_2(x) = 2x^2 - 1$$

$$T_3(x) = 4x^3 - 3x$$

$$T_4(x) = 8x^4 - 8x^2 + 1$$

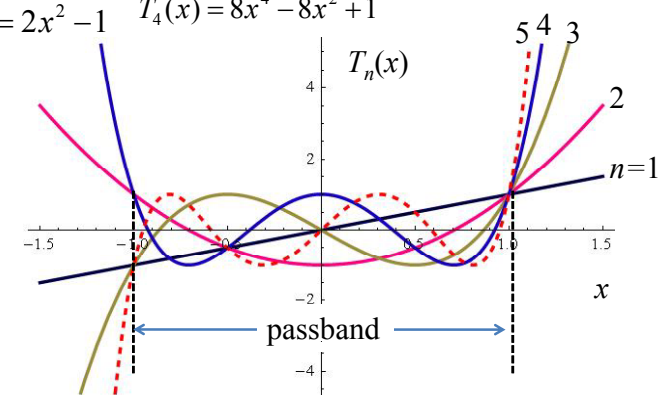
$$T_n(x) = 2xT_{n-1}(x) - T_{n-2}(x) \quad n \geq 2$$



36


5.7 Chebyshev Multisection Matching Transformers

- (1) $|x| \leq 1$, $|T_n(x)| \leq 1$ mapped to passband
Let $x = \cos \theta$, it can be shown that $T_n(\cos \theta) = \cos n\theta$
- (2) $|x| \geq 1$, $|T_n(x)| \geq 1$ outside the passband
- (3) In general, $T_n(x) = \cos(n \cos^{-1} x)$ $|x| \leq 1$
 $= \cosh(n \cosh^{-1} x)$ $|x| \geq 1$

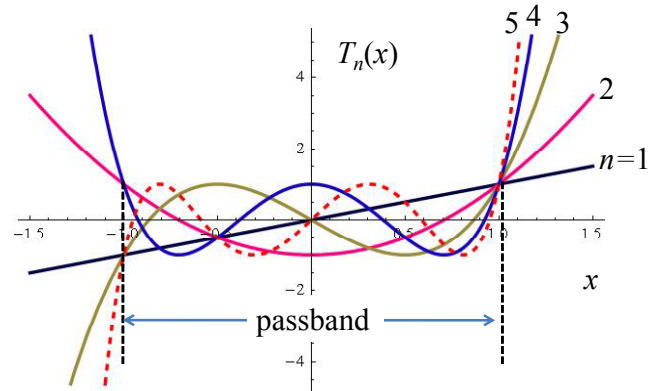


37

Magnitude of Chebyshev Polynomials

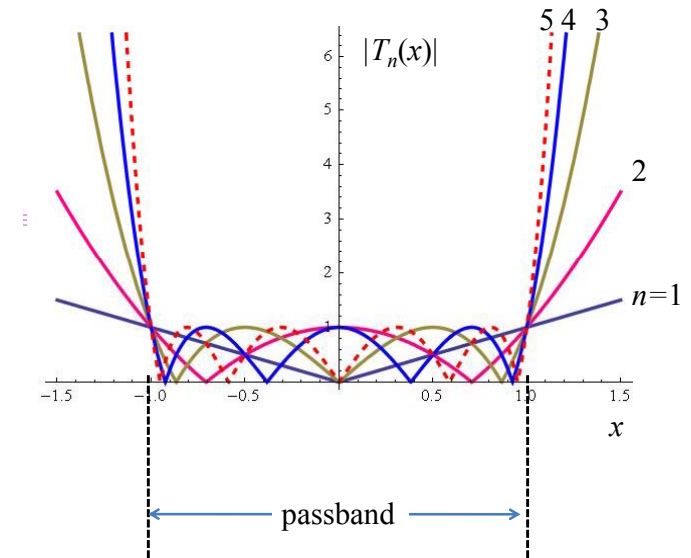


38

Chebyshev Responses

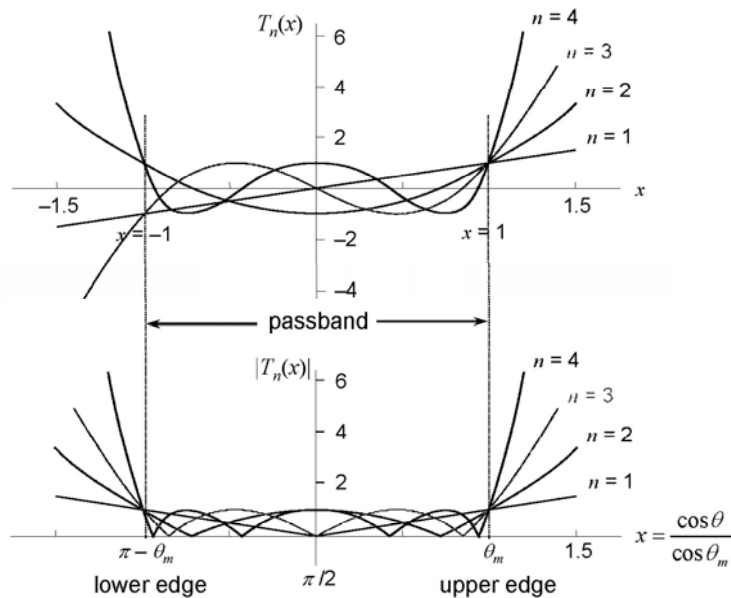

39

Mapping of Passband and Stopband

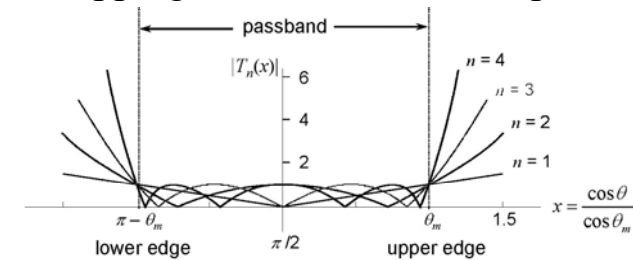

Define $x = \cos \theta / \cos \theta_m \Rightarrow |x| \leq 1$ is mapped to passband
 $\theta_m \Rightarrow x = 1$, the upper passband edge
 $\pi - \theta_m \Rightarrow x = -1$, the lower passband edge

$$T_n(x) = \cos n[\cos^{-1}(\cos \theta / \cos \theta_m)] = T_n(\sec \theta_m \cos \theta)$$

$$T_1(\sec \theta_m \cos \theta) = \sec \theta_m \cos \theta$$


$$T_2(\sec \theta_m \cos \theta) = \sec^2 \theta_m (1 + \cos 2\theta) - 1$$

$$T_3(\sec \theta_m \cos \theta) = \sec^3 \theta_m (\cos 3\theta + 3 \cos \theta) - 3 \sec \theta_m \cos \theta$$

$$T_4(\sec \theta_m \cos \theta) = \sec^4 \theta_m (\cos 4\theta + 4 \cos 2\theta + 3) - 4 \sec^2 \theta_m (1 + \cos 2\theta) + 1$$

40

Design of Chebyshev Transformer

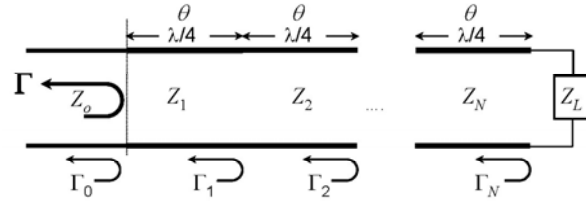

$$\Gamma(\theta) = 2e^{-jN\theta} [\Gamma_0 \cos N\theta + \Gamma_1 \cos(N-2)\theta + \dots + \Gamma_n \cos(N-2n)\theta + \dots]$$

$$\Gamma(0) = \frac{Z_L - Z_0}{Z_L + Z_0} = AT_N(\sec \theta_m) \Rightarrow A = \frac{1}{T_N(\sec \theta_m)} \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma_m = |A| T_N(\cos \theta_m \sec \theta_m) = |A|$$

$$T_N(\sec \theta_m) = \frac{1}{A} \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{1}{\Gamma_m} \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right|, \quad \sec \theta_m = \cosh \left[\frac{1}{N} \cosh^{-1} \left(\frac{1}{\Gamma_m} \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right| \right) \right]$$

$$\frac{\Delta f}{f_0} = 2 - \frac{4\theta_m}{\pi}$$

41

Table 5.2 Chebyshev Transformer Design

Z_L/Z_0	$N = 2$				$N = 3$			
	$\Gamma_m = 0.05$		$\Gamma_m = 0.20$		$\Gamma_m = 0.05$		$\Gamma_m = 0.20$	
	Z_1/Z_0	Z_2/Z_0	Z_1/Z_0	Z_2/Z_0	Z_1/Z_0	Z_2/Z_0	Z_3/Z_0	Z_1/Z_0
1.0	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000
1.5	1.1347	1.3219	1.2247	1.2247	1.1029	1.2247	1.3601	1.2247
2.0	1.2193	1.6402	1.3161	1.5197	1.1475	1.4142	1.7429	1.2855
3.0	1.3494	2.2232	1.4565	2.0598	1.2171	1.7321	2.4649	1.3743
4.0	1.4500	2.7585	1.5651	2.5558	1.2662	2.0000	3.1591	1.4333
6.0	1.6047	3.7389	1.7321	3.4641	1.3383	2.4495	4.4833	1.5193
8.0	1.7244	4.6393	1.8612	4.2983	1.3944	2.8284	5.7372	1.5766
10.0	1.8233	5.4845	1.9680	5.0813	1.4385	3.1623	6.9517	1.6415

Z_L/Z_0	$N = 4$				$\Gamma_m = 0.20$			
	$\Gamma_m = 0.05$				Z_1/Z_0	Z_2/Z_0	Z_3/Z_0	Z_4/Z_0
	Z_1/Z_0	Z_2/Z_0	Z_3/Z_0	Z_4/Z_0	Z_1/Z_0	Z_2/Z_0	Z_3/Z_0	Z_4/Z_0
1.0	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000	1.0000
1.5	1.0892	1.1742	1.2775	1.3772	1.2247	1.2247	1.2247	1.2247
2.0	1.1201	1.2979	1.5409	1.7855	1.2727	1.3634	1.4669	1.5715
3.0	1.1586	1.4876	2.0167	2.5893	1.4879	1.5819	1.8965	2.0163
4.0	1.1906	1.6414	2.4369	3.3597	1.3692	1.7490	2.2870	2.9214
6.0	1.2290	1.8773	3.1961	4.8820	1.4415	2.0231	2.9657	4.1623
8.0	1.2583	2.0657	3.8728	6.3578	1.4914	2.2428	3.5670	5.3641
10.0	1.2832	2.2268	4.4907	7.7930	1.5163	2.4210	4.1305	6.5950

42

Example 5.6

Design a Chebyshev transformer of $N=3$ for $Z_L = 2Z_0 = 100 \Omega$ with $\Gamma_m = 0.05$.

Sol: $\Gamma(\theta) = 2e^{-j3\theta} [\Gamma_0 \cos 3\theta + \Gamma_1 \cos \theta]$

$$= Ae^{-j3\theta} T_3(\sec \theta_m \cos \theta)$$

$$= A \sec^3 \theta_m (\cos 3\theta + 3 \cos \theta) - 3A \sec \theta_m \cos \theta$$

$$A = \Gamma_m = 0.05$$

$$\sec \theta_m = \cosh \left[\frac{1}{N} \cosh^{-1} \left(\frac{1}{\Gamma_m} \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right| \right) \right]$$

$$= \cosh \left[\frac{1}{3} \cosh^{-1} \left(\frac{20}{3} \right) \right] = 1.408$$

$$2\Gamma_0 = A \sec^3 \theta_m \Rightarrow \Gamma_0 = 0.0698 = \Gamma_3$$

$$2\Gamma_1 = 3A(\sec^3 \theta_m - \sec \theta_m) \Rightarrow \Gamma_1 = 0.1037 = \Gamma_2$$

43

Example 5.6


Design a Chebyshev transformer of $N=3$

$$Z_1 = Z_0 \frac{1 + \Gamma_0}{1 - \Gamma_0} = 57.50 \Omega$$

$$Z_2 = Z_1 \frac{1 + \Gamma_1}{1 - \Gamma_1} = 70.81 \Omega$$


$$Z_3 = Z_2 \frac{1 + \Gamma_2}{1 - \Gamma_2} = 87.20 \Omega$$

$$\frac{\Delta f}{f_0} = 2 - \frac{4\theta_m}{\pi} \Big|_{\theta_m=44.7^\circ} = 101\%$$

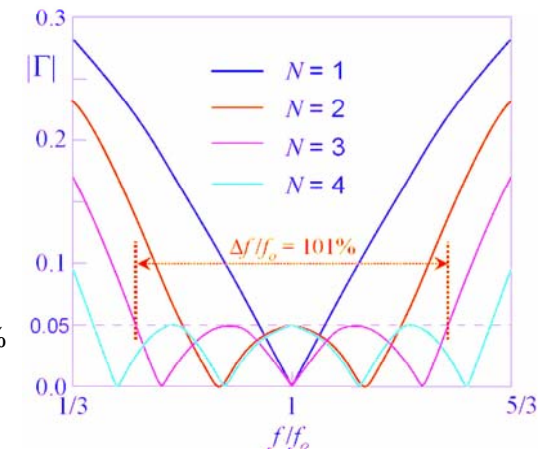

44

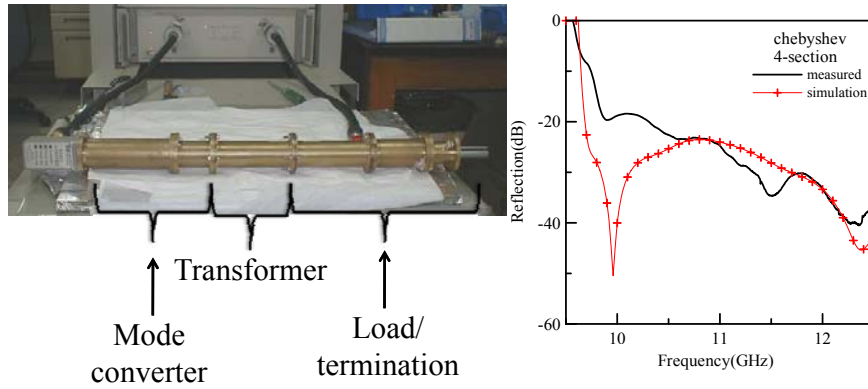Example: “Chebyshev轉換器特性之深入探討電腦模與實驗量測” 清大物理 碩士論文 張靜宜



Chebyshev四階轉換器電腦模擬與實驗結果之比較

45

The End of Chap. 5

46